



Hardware Programming

HWP01

2020-2021

capturing a

FPGA

design with

VHDL

Planning: theory

- First week
 - Introduction digital systems
 - Introduction to FPGAs
 - Structured digital Design
 - Modeling concepts in VHDL
- Second Week
 - Introduction VHDL
 - Code structure
 - Data types
- Third week
 - Combinational versus sequential design
 - Concurrent and sequential code
 - Signals and variables
- Fourth week
 - Introduction to state machines
- Fifth week
 - Designing state machines
 - Advanced VHDL design

Agenda

- Introduction to VHDL
- Code structure and data types
- Design verification

Introduction to VHDL

- VHSIC was a 1980s U.S. government program to develop very-high-speed integrated circuits. The United States Department of Defense launched the VHSIC project in 1980 as a joint tri-service project. The project led to advances in integrated circuit materials, lithography, packaging, testing, and algorithms, and created numerous computer-aided design tools. A well-known part of the project's contribution is VHDL, a hardware description language.
- Standard defined by IEEE in 1987
- Remember: VHDL is not a normal programming language
- Everything happens all the time

VHDL Design

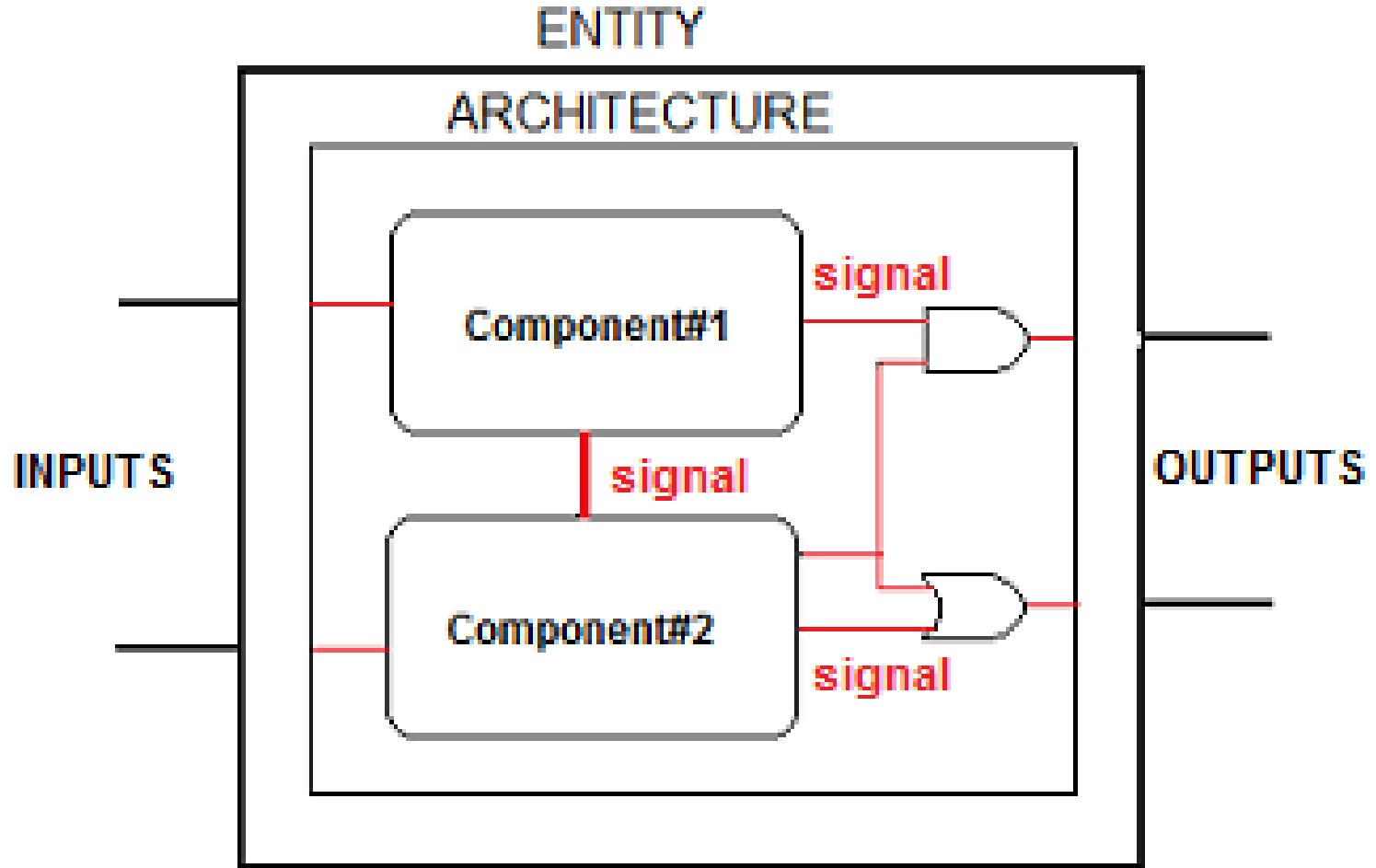


Figure adapted from FPGAcenter.com

Entity and architecture keywords

- **ENTITY**

- Define a function block and specify the interface to the outside world with **PORTS**

- **ARCHITECTURE**

- Define the implementation of your entity. Either behavioral or structural

Design verification: test bench

- Functional verification of your design
- In this course you will have to create a test bench for every assignment you hand in

 


Figure adapted from Duckworth.

Test bench overview

- A test bench entity has no ports
- In the architecture you create port maps to instantiate your design
- Generate a clock signal as stimulus
- In this course we only cover functional verification; no timing verification

Delay models

- Inertial delay:
 - Models delays in gates with the after clause: **a <= b AFTER 1 ns;**
- Transport delay:
 - Models delays in wires
- Delta delay:
 - Delay added automatically by the simulator if no delay is explicitly prescribed
- Remember: delay statements are **not** synthesizable

Discussion of example

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
USE ieee.numeric_std.all;

ENTITY assignment2_tb IS
END ENTITY;

ARCHITECTURE testbench OF assignment2_tb IS
    COMPONENT assignment2 IS
        PORT (
            SW          : IN STD_LOGIC_VECTOR(17 DOWNTO 0);
            HEX0        : IN STD_LOGIC_VECTOR(6 DOWNTO 0);
            LEDR        : IN STD_LOGIC_VECTOR(17 DOWNTO 0)
        );
    END COMPONENT;
    SIGNAL SW_tb          : STD_LOGIC_VECTOR(17 DOWNTO 0);
    SIGNAL HEX0_tb        : STD_LOGIC_VECTOR(6 DOWNTO 0);
    SIGNAL LEDR_tb        : STD_LOGIC_VECTOR(17 DOWNTO 0);

    BEGIN
TB: assignment2 PORT MAP (SW => SW_tb, HEX0 => HEX0_tb, LEDR => LEDR_tb);
PROCESS
BEGIN
    SW_tb <= "000000000000000000";
    FOR I IN 0 TO 15 LOOP
        WAIT FOR 10 ns;
        SW_tb <= STD_LOGIC_VECTOR(UNSIGNED(SW_tb) + 1);
    END LOOP;


    REPORT "Test completed.";
    WAIT;
END PROCESS;

END ARCHITECTURE;
```

Agenda

- Introduction to VHDL
- **Code structure and data types**
- Design verification

Example: AND gate

 

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY andgate IS  
    PORT (a,b: IN  STD_LOGIC;  
          c: OUT STD_LOGIC);  
END andgate;  
-----  
ARCHITECTURE voorbeeld OF andgate IS  
BEGIN  
    c <= A AND B;  
END voorbeeld;  
-----
```

- -----
- `LIBRARY library_name;`
- `USE library_name.package_name.all;`
- -----

The most frequently used packages are:

- Package *standard*, from the library *std* (visible by default)
- Library *work* (where the projects are saved is visible by default)
- Package *std_logic_1164*, from the library *ieee* (when needed, must be explicitly declared)

- -----
- `LIBRARY std; -- optional declaration`
- `USE std.standard.all; --optional`
- `LIBRARY work -- optional`
- `USE work.all -- optional; also not needed if defined as below`
- `USE work.my_package.all; --if an extra user made package is needed`
- `LIBRARY ieee;`
- `USE ieee.std_logic_1164.all`
- -----

INCLUDE : *IEEE.STD_LOGIC_1164* LIBRARY

https://www.csee.umbc.edu/portal/help/VHDL/std_logic_1164.vhdl

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----
```

Defines STD_LOGIC as well as STD_LOGIC_VECTOR (array of STD_LOGIC)

- 'U', -- Uninitialized
- 'X', -- Unknown
- '0', -- LOGIC 0
- '1', -- LOGIC 1
- 'Z', -- High Impedance (used for tri-state I/O's)
- 'W', -- Weak signal
- 'L', -- Weak signal with logic 0 as preference
- 'H', -- Weak signal with logic 1 as preference
- '-' -- Don't care

Defines various FUNCTIONS, such as EDGE DETECTION

```
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN;  
FUNCTION falling_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN;
```

INCLUDE : *IEEE.STD_LOGIC_1164* LIBRARY

https://www.csee.umbc.edu/portal/help/VHDL/std_logic_1164.vhdl

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----
```

Defines STD_LOGIC as well as STD_LOGIC_VECTOR (array of STD_LOGIC)

- 'U', -- Uninitialized
- 'X', -- Unknown
- '0', -- LOGIC 0
- '1', -- LOGIC 1
- 'Z', -- High Impedance (used for tri-state I/O's)
- 'W', -- Weak signal
- 'L', -- Weak signal with logic 0 as preference
- 'H', -- Weak signal with logic 1 as preference
- '-' -- Don't care

Defines various FUNCTIONS, such as EDGE DETECTION

```
-----  
FUNCTION rising_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN;  
FUNCTION falling_edge (SIGNAL s : std_ulogic) RETURN BOOLEAN;
```

Data Types: IEEE 1164 Standard Logic

- IEEE's **std_logic_1164** examples:

- STD_LOGIC

```
SIGNAL a: STD_LOGIC;  
  
a <= '0';      -- a is zero  
a <= '1';      -- a is one  
a <= 'Z';      -- a is high-impedance  
                -- used for bidi ports
```

- STD_LOGIC_VECTOR

```
SIGNAL b: STD_LOGIC_VECTOR (7 DOWNT0 0);  
  
b <= "1100ZZZZ"; -- array of 8 std_logic's  
                -- in MSB representation
```


Data Types: *IEEE.numeric_std.all* LIBRARY

```
-----  
LIBRARY ieee;  
USE ieee.numeric_std.all;  
-----
```

Allows for: unsigned, signed, integer, natural

Contains many **functions** such as: abs(), + addition, - subtraction, * multiplication, / division, etc..., that can be used with these types

As well as: >, <, <=, >=, =, SHIFT_LEFT, SHIFT_RIGHT

Normal STD_LOGIC_VECTORS: can't calculate with those!

Additional **Type conversion functions** needed to overcome this.....

https://www.csee.umbc.edu/portal/help/VHDL/numeric_std.vhdl

Conversion of Common Types

```
SIGNAL a: STD_LOGIC_VECTOR(7 DOWNT0 0);  
SIGNAL b: UNSIGNED (7 DOWNT0 0);  
SIGNAL c: SIGNED (7 DOWNT0 0);
```

(un)signed → std_logic_vector

```
a <= STD_LOGIC_VECTOR(b);  
a <= STD_LOGIC_VECTOR(c);
```

std_logic_vector → (un)signed

```
b <= UNSIGNED(a);  
c <= SIGNED(a);
```

Conversion of Common Types

```
SIGNAL d: UNSIGNED (7 DOWNT0 0);  
SIGNAL e: SIGNED (7 DOWNT0 0);  
SIGNAL f: INTEGER RANGE 0 TO 255;  
SIGNAL g: INTEGER RANGE -128 TO 127;
```

integer → (un)signed

```
d <= TO_UNSIGNED(f, 8);      -- d is an array of 8  
e <= TO_SIGNED(g, 8);       -- e is an array of 8
```

(un)signed → integer

```
f <= TO_INTEGER(d);  
g <= TO_INTEGER(e);
```

Conversion of Common Types

```
SIGNAL h: STD_LOGIC_VECTOR (7 DOWNT0 0);  
SIGNAL i: INTEGER RANGE 0 TO 255;  
SIGNAL j: INTEGER RANGE -128 TO 127;
```

integer → std_logic_vector

```
h <= STD_LOGIC_VECTOR(TO_UNSIGNED(i,8));  
h <= STD_LOGIC_VECTOR(TO_SIGNED(j,8));
```

std_logic_vector → integer

```
i <= TO_INTEGER(UNSIGNED(h));  
j <= TO_INTEGER(SIGNED(h));
```

Warning

STD_LOGIC_ARITH
is
OBSOLETE

Don't use it, no matter what older books or websites/forums/code snippets online say!

Use IEEE 1164

ieee.numeric_std.all

instead for unsigned and signed types!

Assignment Operators

- `<=` for a *signal*
- `:=` for a *variable* (covered later)
- `=>` for individual elements of a vector

Example:

```
signal    a: std_logic;
variable b: integer range 0 to 255;
signal    c: std_logic_vector(3 downto 0);

a <= '1';                                -- assign single bits with '
b := 10;                                  -- assign an integer
c <= "1100";                              -- assign a vector with "
c <= (3 => '1', 2 => '1', OTHERS => '0'); -- same as previous line
a <= c(0);
```

Other Functions available with numeric_std

- Logical

NOT, AND, OR, NAND, NOR, XOR, XNOR

- Arithmetic

+, -, *, /, **, MOD, REM, ABS

NOTE: Not all synthesizable

- Comparison

=, /=, <, >, <=, >=

- Shift operators:

sll, srl -- shift left logical, shift right logical

sla, sra -- shift right arithmetic, shift right arithmetic

rol, ror -- rotate left, rotate right

Attributes

```
SIGNAL d : STD_LOGIC_VECTOR (7 DOWNT0 0) ;
```

```
d'LOW      = 0          -- laagste array index
d'HIGH     = 7          -- hoogste array index
d'LEFT     = 7          -- meest linkse array index
d'RIGHT    = 0          -- meest rechtse array index
d'LENGTH   = 8          -- lengte van de vector
d'RANGE    = (7 DOWNT0 0) -- range of the vector
d'REVERSE_RANGE = (0 TO 7) -- reverse range of the vector
```


Signal Attributes

- ***Most*** signal attributes are ***not synthesizable***. They are used primarily for simulation.
- Attributes of enumeration types should not be used for synthesis, nor should the attributes POS, VAL, SUCC, PRED, LEFTOF, RIGHTOF.
- Many synthesis tools do not support these particular attributes, and attributes of enumeration types can become invalid during optimization.
- Use standard expressions **rising_edge(clk)**.

Simple Signal Assignment statement

- When the Right Hand Side (RHS) of a signal assignment changes the signal assignment statement is executed
- Signals in a circuit are modeled as signal statement assignments in VHDL
- Order in text is *not* preserved!

Example: DFF (bad)

- In many code snippets people use 'EVENT like this:

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY dff IS  
    PORT (d, clk, rst: IN  STD_LOGIC;  
          q, qi      : OUT STD_LOGIC);  
END dff;  
-----  
ARCHITECTURE implementation OF dff IS  
BEGIN  
    PROCESS (rst, clk)  
    BEGIN  
        IF (rst='1') THEN  
            q <= '0';  
        ELSIF (clk'EVENT AND clk='1') THEN  
            q <= d;  
        END IF  
    END PROCESS;  
    qi <= NOT(q);  
END implementation;
```

Why is this not a proper DFF?

Hint: think of the values a STD_LOGIC signal can obtain by definition...



Example: DFF (good)

- Use rising_edge() function (or falling_edge())

```
-----  
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
-----  
ENTITY dff IS  
    PORT(d, clk, rst: IN STD_LOGIC;  
         q, qi: OUT STD_LOGIC)  
END dff;  
-----  
ARCHITECTURE dff_arch OF dff IS  
BEGIN  
    PROCESS (rst, clk)  
    BEGIN  
        IF (rst='1') THEN  
            q <= '0';  
        ELSIF rising_edge(clk)  
        THEN  
            q <= d;  
        END IF;  
    END PROCESS;  
  
    qi <= NOT(q);  
  
END dff_arch;
```


- Looks like this
in the library:

```
FUNCTION rising_edge (SIGNAL s : std_ulogic)  
RETURN BOOLEAN IS  
BEGIN  
    RETURN (s'EVENT AND (To_X01(s) = '1')  
            AND (To_X01(s'LAST_VALUE) = '0'));  
END;
```

- Make sure it is a real
rising edge from 0 to 1,
and not from X or Z.

D flip-flop

 - We'll show you a behavioral and structural description of a simple D flip-flop




$Q =$
0 if clear=1,
I if load=1 and clock=1,
Q(previous) otherwise.

Figures adapted from Embedded Systems Design: A Unified Hardware/Software Introduction

Behavioral D flip-flop

```
-----  
entity dff is  
Port ( data_in:      in std_logic;  
        clock:        in std_logic;  
        data_out:     out std_logic  
);  
end dff;  
-----  
architecture behv of dff is  
begin  
    process(clock)  
    begin  
        -- clock rising edge  
  
        if rising_edge(clock) then  
            data_out <= data_in;  
        end if;  
  
    end process;  
end behv;  
-----
```

Structural D flip-flop

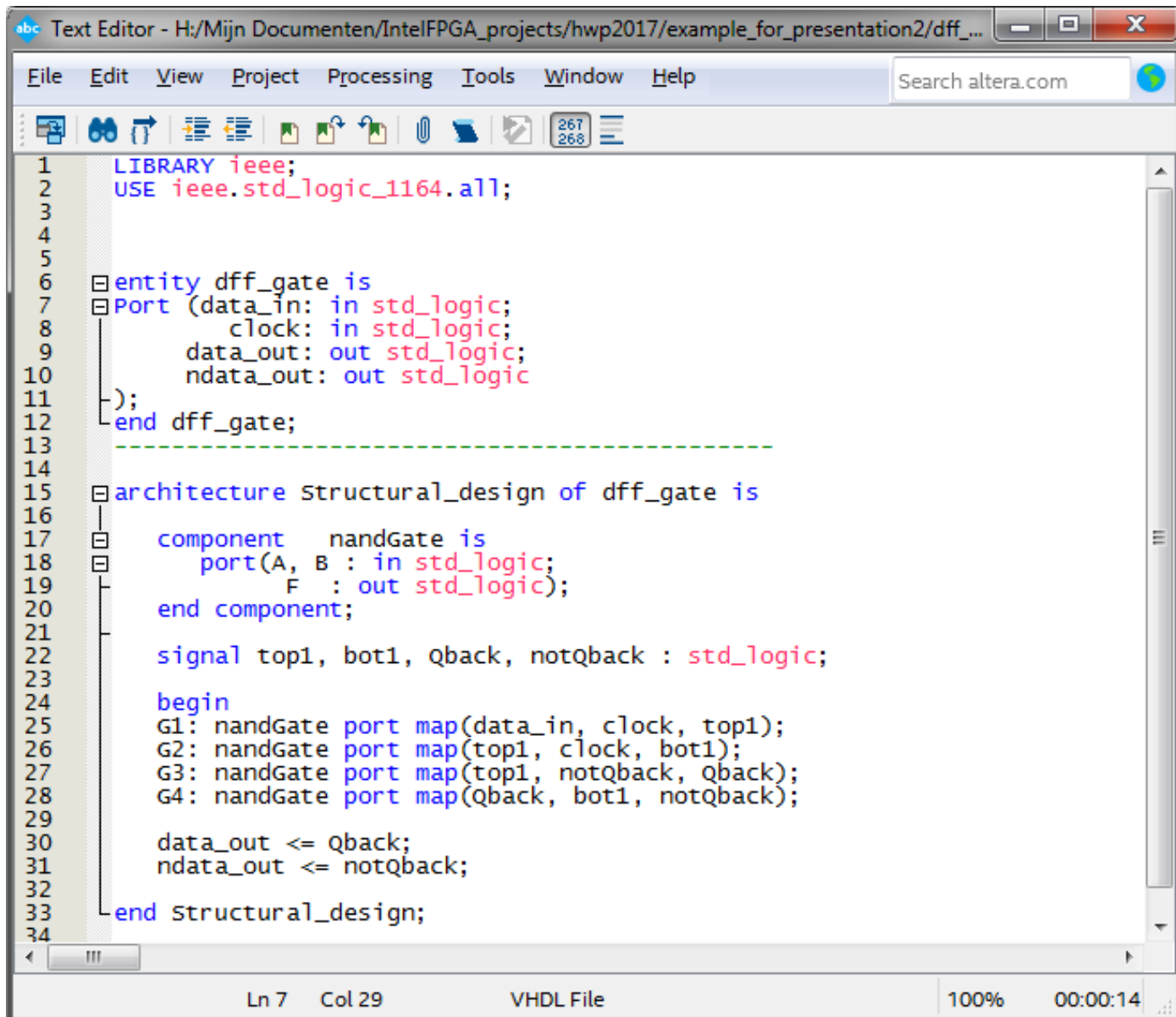

The image shows a screenshot of a text editor window titled "Text Editor - H:/Mijn Documenten/IntelFPGA_projects/hwp2017/example_for_presentation2/dff_...". The editor contains VHDL code for a structural D flip-flop. The code is as follows:

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4
5
6  entity dff_gate is
7  port (data_in: in std_logic;
8        clock: in std_logic;
9        data_out: out std_logic;
10       ndata_out: out std_logic
11  );
12  end dff_gate;
13  -----
14
15  architecture Structural_design of dff_gate is
16  component nandGate is
17  port (A, B : in std_logic;
18        F : out std_logic);
19  end component;
20
21  signal top1, bot1, Qback, notQback : std_logic;
22
23  begin
24  G1: nandGate port map(data_in, clock, top1);
25  G2: nandGate port map(top1, clock, bot1);
26  G3: nandGate port map(top1, notQback, Qback);
27  G4: nandGate port map(Qback, bot1, notQback);
28
29  data_out <= Qback;
30  ndata_out <= notQback;
31
32  end Structural_design;
```

The editor interface includes a menu bar (File, Edit, View, Project, Processing, Tools, Window, Help), a search bar (Search altera.com), and a toolbar with various icons. The status bar at the bottom shows "Ln 7 Col 29", "VHDL File", "100%", and "00:00:14".

Agenda

- Discussion of previous week
- Introduction to VHDL
- Code structure and data types
- **Design verification**

VHDL Golden Reference

- The VHDL Golden Reference Guide by DOULOS
- Use it as a reference
- Link:
http://www.ics.uci.edu/~jmoorkan/vhdlref/vhdl_golden_reference_guide.pdf

Summary

- Behavioral and structural design
- Use standard functions for conversion of data types
- Verify the functional behavior of your design with test benches

Homework

- Covered today:
 - Discussion of previous week
 - Introduction to VHDL
 - Code structure and data types
 - Design verification
- Homework:
 - 2.1, 2.2a, 3.1, 3.20, 3.22, 3.24
- Next week:
 - Combinational versus sequential design
 - Concurrent and sequential code
 - Signals versus variables