



Hardware Programming

HWP01

2020-2021

capturing a

FPGA

design with

VHDL

Planning: theory


- First week
 - Introduction digital systems
 - Structured digital Design
 - RTL
- Second week
 - Introduction VHDL
 - Code structure and data types
 - Design verification
- **Third week**
 - Combinational versus sequential design
 - Concurrent and sequential code
 - Signals and variables
- Fourth week
 - Introduction to state machines
- Fifth week
 - Designing state machines
 - Advanced VHDL design

Agenda

- **Discussion of previous week**
- Combinational versus sequential design
- Concurrent and sequential code
- Signals versus variables

Numbers

Bit Vectors

 


Zie ook:
TABEL:
H.3 ; blz 76

Agenda

- Discussion of previous week
- **Combinational versus sequential design**
- Concurrent and sequential code
- Signals versus variables

Combinational and sequential logic (1/2)


- Combinational: **no** memory

 

- The output is a function only of the current inputs.
- In any implementation there is a ***propagation delay***
 - For this course, we pretend the propagation delay is zero (except for one assignment).

Combinational and sequential logic (2/2)



- Sequential logic:

 

- The output of sequential logic, is ...
... a function of a *sequence* of operations ..
... on current and/or *previous inputs*.
- Advantages?



Combinational vs. sequential logic example

- Combinational

  

Updates instantly
as input changes
(in theory).

- Sequential

  

Updates
only when
CLK goes
high. Until
then it
remembers
the
previous
input
(memory)

Combinational or sequential?

- Multiplexer vs. Gated-Multiplexer?
- Timer?
- Encoder (for example binary to 7-seg display)?
- Comparators?
- Adder?
- Multiplier?
- ALU?
- CPU?
- RAM?


Agenda

- Discussion of previous week
- Combinational versus sequential design
- **Concurrent and sequential code**
- Signals versus variables

Concurrent Code

- Concurrent code is intended **only for combinational circuits**.
 - Often used for structural descriptions of a circuit.
- Outputs activated asynchronously, at any time.
- Statements for concurrent code:
 - **WHEN ... ELSE**
 - **WITH ... SELECT**
 - **GENERATE**
- Can be placed outside **PROCESS**, **FUNCTION** and **PROCEDURE**

WHEN/ELSE

 


```
ARCHITECTURE mux1 OF mux IS
BEGIN
    y <= a WHEN sel="00" ELSE
        b WHEN sel="01" ELSE
        c WHEN sel="10" ELSE
        d;
END mux1;
```

- Read: when sel is equal to "00", y obtains the value of a, else when sel is equal to "01", y obtains the value of b, etc...
- Cover all combinations
- Let the synthesizer do the K-map for us!

WITH/SELECT

 - **WITH ... SELECT** is used very often
- Read: depending on sel, y becomes a when sel is 00, y becomes b when sel is 01, etc...
- Note the usage of the **OTHERS** keyword here to cover *all* possibilities



```
ARCHITECTURE mux2 OF mux IS
BEGIN
    WITH sel SELECT
        y <= a WHEN "00",      -- Use "," not ";"
            b WHEN "01",
            c WHEN "10",
            d WHEN OTHERS;
END mux2;
```


Gated Multiplexer

```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
  
-----  
ENTITY gated_mux IS  
    PORT (a, b, c, d, clk: IN STD_LOGIC;  
          sel      : IN  STD_LOGIC_VECTOR (1 DOWNTO 0);  
          x, y      : OUT STD_LOGIC);  
END gated_mux;
```

```
-----  
ARCHITECTURE behavioral OF gated_mux IS  
BEGIN
```

```
    WITH sel SELECT  
        x <= a WHEN "00",      -- Use "," not ";"  
        b WHEN "01",  
        c WHEN "10",  
        d WHEN OTHERS;
```



 
```
PROCESS (clk)  
BEGIN  
    IF rising_edge(clk) THEN  
        y <= x;  
    END IF  
END PROCESS  
END ARCHITECTURE
```



Sequential Code

- Statements for sequential code:
 - IF
 - WAIT
 - FOR x IN 0 TO 10 LOOP
 - CASE
- Sequential code can be used to design both **sequential *and* combinational** circuits
- Code within a **PROCESS**, **FUNCTION** or **PROCEDURE** is sequential.


Sequential Code Circuit Examples

   

Sequential Code

- **PROCESS** is a *sequential* section, located in the **ARCHITECTURE**
- Note that multiple processes are allowed. They are *concurrent* to each other.
- *ONLY* support for the following *sequential* statements:
 - **IF**
 - **WAIT**
 - **LOOP**
 - **CASE**

Multiplexer with sequential code

 

- A **PROCESS** has a **sensitivity list**
- The outputs of the **PROCESS** get updated if the value of an object in the list changes

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY seq_code_mux IS
    PORT (a, b, c, d: IN  STD_LOGIC;
          sel       : IN  STD_LOGIC_VECTOR (1 DOWNTO 0);
          y         : OUT STD_LOGIC);
END seq_code_mux;

-----

ARCHITECTURE seq_code_impl OF seq_code_mux IS
BEGIN

    PROCESS (sel, a, b, c, d)
    BEGIN

        IF      sel = "00" THEN
            y <= a;
        ELSIF  sel = "01" THEN
            y <= b;
        ELSIF  sel = "10" THEN
            y <= c;
        ELSE
            y <= d;
        END IF;

    END PROCESS;

END seq_code_impl;
```

Multiplexer with CASE

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----


ENTITY seq_code_mux IS
    PORT (a, b, c, d: IN  STD_LOGIC;
          sel      : IN  STD_LOGIC_VECTOR (1 DOWNT0 0);
          y        : OUT STD_LOGIC);
END seq_code_mux;

-----


ARCHITECTURE seq_code_impl OF seq_code_mux IS
BEGIN
    PROCESS(sel,a,b,c,d)
    BEGIN
        CASE sel IS
            WHEN "00" =>
                y <= a;
            WHEN "01" =>
                y <= b;
            WHEN "10" =>
                y <= c;
            WHEN OTHERS =>
                y <= d;
        END CASE;
    END PROCESS;
END seq_code_impl;
```

Tech. map of mux with sequential code

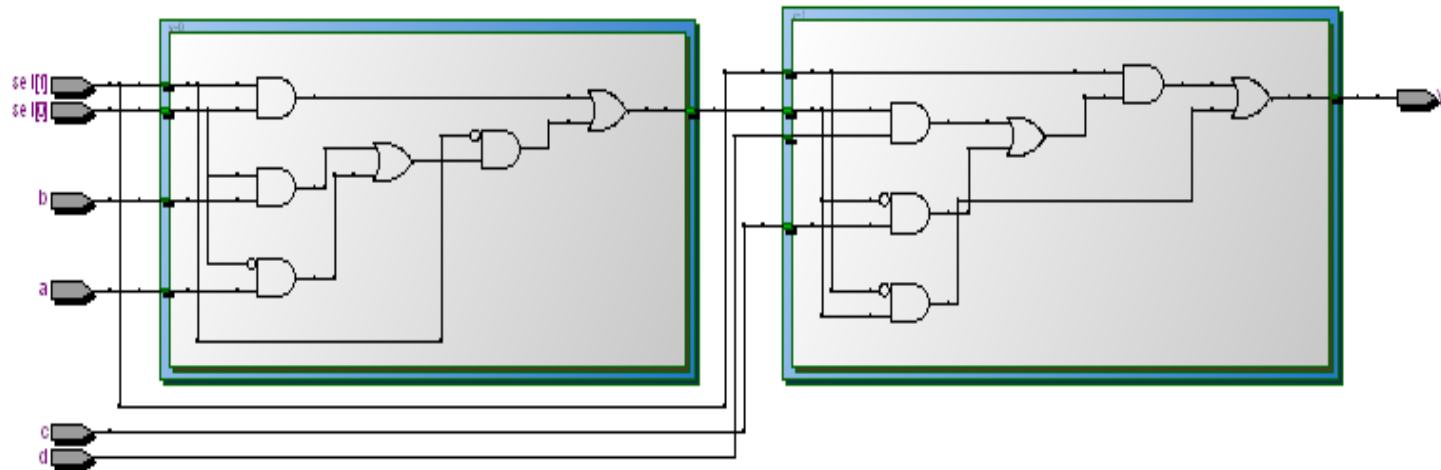Sequential Code can make Combinational Circuits



D Flip-Flop

 

We only want to update Q when the CLK goes high, so only the CLK & R are in the sensitivity list


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----
ENTITY dff_example IS
    PORT (
        clk: IN  STD_LOGIC;
        d,r: IN  STD_LOGIC;
        q  : OUT STD_LOGIC
    );
END dff_example;

-----
ARCHITECTURE dff_implementation OF dff_example IS
BEGIN
    PROCESS(clk, r )
    BEGIN
        IF r = '1' THEN
            q <= '0';
        ELSIF RISING_EDGE(clk) THEN
            q <= d;
        END IF;
    END PROCESS;
END dff_implementation;
```

Technology Map of DFF

 Sequential circuits can only be written with sequential code



Up/down counter

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.numeric_std.ALL;

ENTITY updown IS
    GENERIC (
        COUNTER_WIDTH : INTEGER := 31
    );
    PORT (
        clk             : IN STD_LOGIC;
        rst             : IN STD_LOGIC;

        up_down        : IN STD_LOGIC;

        count_out : OUT UNSIGNED(COUNTER_WIDTH DOWNTO 0)
    );
END updown;
```


Up/down counter

```

ARCHITECTURE arch OF updown IS
    SIGNAL count : UNSIGNED(COUNTER_WIDTH DOWNT0 0);
BEGIN
    PROCESS(clk)
    BEGIN
        IF rising_edge(clk) THEN
            IF rst = '1' THEN
                count <= (OTHERS => '0');
            ELSE
                IF up_ndown = '1' THEN
                    count <= count + 1;
                ELSE
                    count <= count - 1;
                END IF;
            END IF;
        END IF;
    END PROCESS;

    count_out <= count;
END arch;

```

 

WAIT

- In a **PROCESS** you can use the **WAIT** keyword
- A process CANNOT have both a sensitivity list and **WAIT** statements
- Three types:
 - **WAIT UNTIL** <signal>
 - **WAIT ON** sig1, sig2, ..., sign
 - **WAIT FOR** *time*
- **WAIT FOR** cannot be synthesized; only for simulation and test benches

D Flip-Flop with WAIT


```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

-----

ENTITY dff_example IS
    PORT (
        clk: IN  STD_LOGIC;
        d,r: IN  STD_LOGIC;
        q  : OUT STD_LOGIC
    );
END dff_example;

-----

 ARCHITECTURE dff_implementation OF dff_example IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL RISING_EDGE(clk);
        q <= d;
    END PROCESS;
END dff_implementation;
```



Not very
handy without
a reset ☹

Loops in VHDL

- **FOR** and **WHILE** loops
- **FOR ... LOOP** repeats until the upperbound is reached
- Static bounds; use constants to specify the upper bound of your loop

```
PROCESS (sel)
  ..
  BEGIN
    FOR i IN 0 to 5 LOOP
      x <= i;
    END LOOP;
  END PROCESS;
```

Loops in VHDL

- **WHILE ... LOOP** is similar in structure as the **FOR ... LOOP**
- See page 161 of your book for some examples with loops

```
PROCESS(sel)
..
BEGIN
  WHILE(i<10) LOOP
    ...do something...
  END LOOP;
END PROCESS;
```

Agenda

- Discussion of previous week
- Combinational versus sequential design
- Concurrent and sequential code
- **Signals versus variables**

Signals versus variables

- **SIGNAL** properties:
 - Can *ONLY* be declared outside a **PROCESS** but can be used within a **PROCESS**
 - Within sequential code the signal is not 'updated immediately' (at the end of the **PROCESS**)
 - Only a *single* assignment is allowed to a signal in the whole code (multiple assignments in **PROCESSES** are fine, but only the last one will be effective!)
- **VARIABLE** properties:
 - Can *ONLY* be declared inside a **PROCESS**
 - Is 'updated immediately' and can be used in the next line of code
 - *Multiple* assignments are not a problem

Signals and Variables in VHDL (1/2)

```
library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity example is
    port (
        clk:    in    std_logic;
        x:      in    std_logic;


        counter_a:    out integer range 0 to 15;
        counter_b:    out integer range 0 to 15;
    );
end example;
```

Signals and Variables in VHDL (2/2)

```
architecture example of example is
    signal a: integer range 0 to 15 := 0;
begin
    process (clk)
        variable b: integer range 0 to 15 := 0;
    begin
        if rising_edge(clk) then
            a <= a + 1;
            b := b + 1;
            if x = '1' then
                a <= a + 1;
                b := b + 1;
            end if;
        end if;
        counter_b <= b;
    end process;
    counter_a <= a;
end example;
```


Variable
can only
be used
inside
the
process!

Example

 

- When x is high
 - The variable counter is counted up twice
 - The signal counter is counted up only once
 - Only the last assignment is effective for a signal

Last signal assignment is only used

 

- Proof:
 - change $a \leq a + 1$
 - to $a \leq a + 3$
- Conclusion
 - Variables are useful when you have to do multiple assignments inside a process

```
if rising_edge(clk) then
    a <= a + 1;
    b := b + 1;
    if x = '1' then
        a <= a + 3;
        b := b + 1;
    end if;
end if;
```

Formally:

\leq is a concurrent statement!

$:=$ is a sequential statement!

Summary

- Combinational versus sequential design: no memory versus memory.
- In VHDL we can model combinational circuits with sequential statements
- Remember the differences between signals and variables

Homework

- Covered today:
 - Discussion of previous week
 - Combinatorial versus sequential design
 - Concurrent and sequential design
 - Signals versus variables
- Homework:
 - 4.4, 4.5, 5.1, 5.9, 6.3
- Next week:
 - Chapter 6 'Sequential Code'
 - Chapter 7 'SIGNAL and VARIABLE'
 - Chapter 9 'FUNCTION and PROCEDURE'